

Design Idea DI-34

TinySwitch-II

5 W Universal Adapter



Application	Device	Power Output	Input Voltage	Output Voltage	Topology
Adapter	TNY266P	5 W	85-265 VAC	5 V	Flyback

Design Highlights

- Simple design: low parts count (23)
- <300 mW no-load without transformer bias winding
- Frequency jittering reduces EMI - meets EN55022 Class B with no Y capacitor: very low primary-to-secondary leakage current
- $\pm 7\%$ output tolerance with simple Zener reference
- High Frequency (132 kHz) operation allows small, low cost EE16 transformer
- Built-in thermal shutdown protection
- ON/OFF digital regulation: No analog control loop to compensate

Operation


Figure 1 is a simple flyback converter utilizing several *TinySwitch-II* built-in features such as switching frequency jittering, thermal shutdown and auto-restart fault protection.

Typical applications are wall mount adapters and other AC/DC applications requiring very low cost and small size. The ability to meet EMI requirements with no Y capacitor makes this circuit ideal for applications requiring low primary-to-secondary leakage currents.

The *TinySwitch-II* frequency jitter feature and transformer construction allow use of a simple filter (L1, L2, C1 and C2) to meet EMI requirements with L2 used to attenuate high frequency EMI in the radiated spectrum (>30 MHz). The circuit also uses a low cost RCD clamp (C7, D5, R3, and R4). Diode D5 is a Glass Passivated (GP) general purpose diode, allowing partial recovery of the leakage energy by recirculating clamp current during the D5 reverse recovery time, thus improving efficiency. Resistor R3 reduces EMI by limiting the peak D5 reverse current and thus softening its recovery characteristic.

The combined voltage drops of Zener diode (VR7) and optocoupler diode (U2) set the output voltage. Resistor R7 biases VR7 according to its specification. The *TinySwitch-II* feedback current is independent of load allowing $\pm 7\%$ output voltage tolerance with this simple Zener reference.

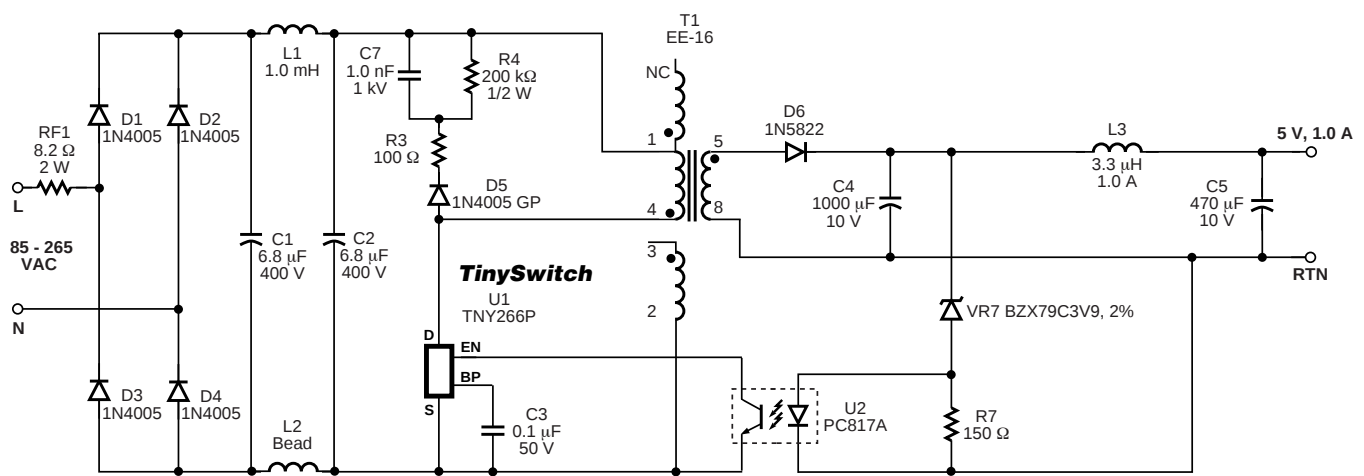Due to the digital nature of the *TinySwitch-II* control scheme, no loop compensation is required. In addition, the current transfer ratio (CTR) of the optocoupler is not critical and no DC gain setting resistor in series with VR7 is required.



PI-3326-051303

Figure 1. *TinySwitch-II* – TNY266P, 5 V, 1 A, 5 W Charger-Adapter Power Supply.

Key Design Points

- Use K_{RP} (ripple-to-peak current ratio) in the range of 0.4 to 0.6 and V_{OR} (output reflected voltage) of 90 V to 110 V for best efficiency.
- Use low cost optocoupler - gain is non-critical.
- PCB traces which carry high switching voltages and current should be short and wide to reduce EMI.
- Reduce leakage inductance by filling each winding layer across the entire width of the bobbin.
- R4 should be large enough to limit dissipation, to meet <300 mW no-load target, while still limiting peak DRAIN voltage to a safe value – 200 k Ω is a good start value for most designs.
- A layer of insulation tape between each layer of primary winding will further reduce inter-winding capacitance and therefore switching losses.
- Ferrite bead L2 reduces radiated EMI.

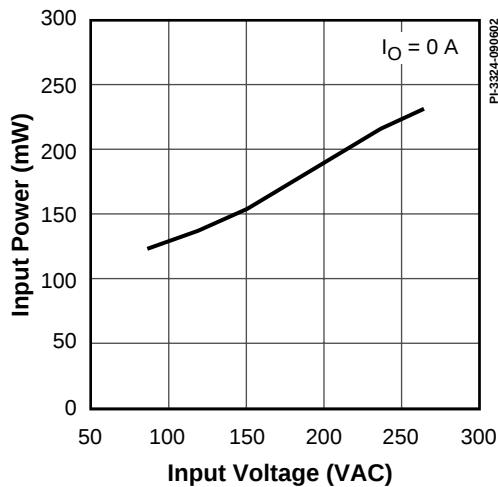


Figure 2. No-load Input Power Consumption.

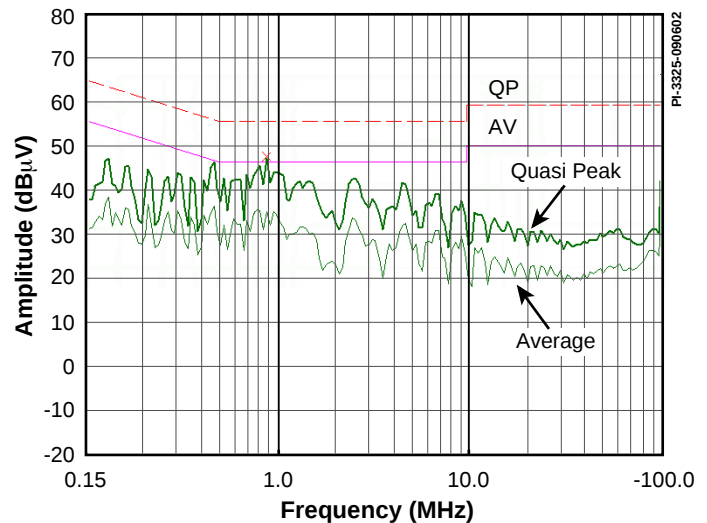


Figure 3. Conducted Emissions-EN55022 Class B (QP and AVG), 5 V, 1 A, 230 VAC, with Artificial Hand Connected to Secondary Return.

TRANSFORMER PARAMETERS

Core	EE16, Nippon Ceramic NC-2H or equivalent, $A_L = 135 \text{ nH/T}^2$
Bobbin	EEL16 Vertical
Winding Order (pin numbers)	Shield (1-NC), Primary (4-1), Shield (3-2), and Secondary (10-8).
Primary Inductance (Pins 1-4 all others open)	1660 $\mu\text{H} \pm 10\%$
Primary Resonant Frequency (Pins 1-4, all other open)	400 kHz (minimum)
Leakage Inductance (Pins 1-4, with Pins 8-14 shorted)	70 μH (maximum)

Table 1. Transformer Design Parameters.

For the latest updates, visit our Web site: www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein, nor does it convey any license under its patent rights or the rights of others. The products and applications illustrated herein (including circuits external to the products and transformer construction) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com.

The PI Logo, **TOPSwitch**, **TinySwitch**, **LinkSwitch** and **EcoSmart** are registered trademarks of Power Integrations, Inc. **PI Expert** is a trademark of Power Integrations, Inc. ©Copyright 2003, Power Integrations, Inc.

WORLD HEADQUARTERS AMERICAS

Power Integrations, Inc.
San Jose, CA 95138 USA
Customer Service:
Phone: +1 408-414-9665
Fax: +1 408-414-9765
e-mail: usasales@powerint.com

CHINA

Power Integrations International Holdings, Inc.
China
Phone: +86-755-8367-5143
Fax: +86-755-8377-9610
e-mail: chinasales@powerint.com

EUROPE & AFRICA

Power Integrations (Europe) Ltd.
United Kingdom
Phone: +44-1344-462-300
Fax: +44-1344-311-732
e-mail: eurosales@powerint.com

KOREA

Power Integrations International Holdings, Inc.
Seoul, Korea
Phone: +82-2-782-2840
Fax: +82-2-782-4427
e-mail: koreasales@powerint.com

SINGAPORE

Power Integrations, Singapore
Republic of Singapore 308900
Phone: +65-6358-2160
Fax: +65-6358-2015
e-mail: singaporesales@powerint.com

JAPAN

Power Integrations, K.K.
Keihin-Tatemono 1st Bldg.
Japan
Phone: +81-45-471-1021
Fax: +81-45-471-3717
e-mail: japansales@powerint.com

APPLICATIONS HOTLINE

World Wide +1-408-414-9660

TAIWAN

Power Integrations International Holdings, Inc.
Taipei, Taiwan
Phone: +886-2-2727-1221
Fax: +886-2-2727-1223
e-mail: taiwansales@powerint.com

INDIA (Technical Support)

Innovatech
Bangalore, India
Phone: +91-80-226-6023
Fax: +91-80-228-9727
e-mail: indiasales@powerint.com

APPLICATIONS FAX

World Wide +1-408-414-9760