

Figure 2. An Ultra-Low-Power Op Amp Offers Simple, Positive Polarity Output to Support a Zero Bias Condition

For a more comprehensive assessment, the circuit in Fig. 3 tests the solar source to see if it can handle the load. The circuit shown makes this assessment without burdening the microcontroller and risking collapse of the supply during measurement.

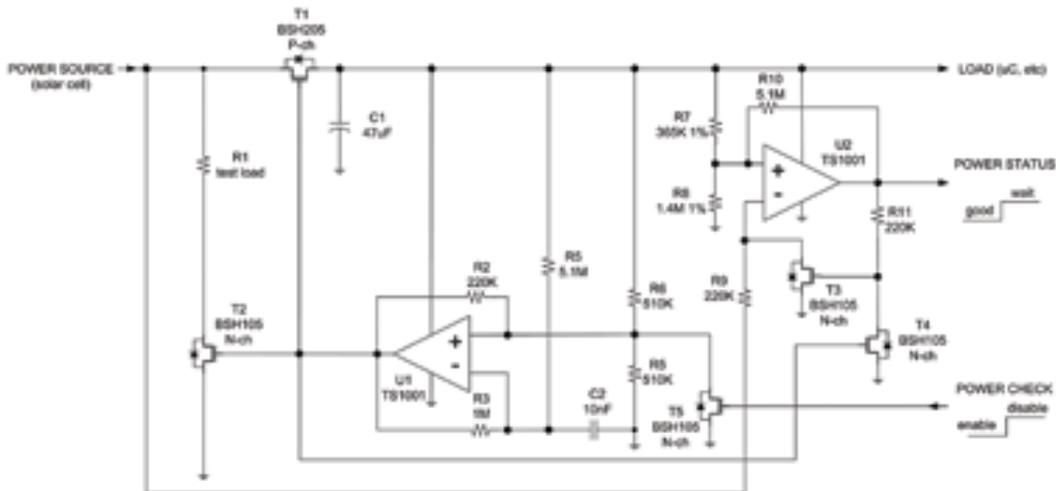


Figure 3. An Ultra-Low-Power Op-Amp-based Circuit Assesses A Pv Solar-Cell Source

Approximately once per 100 ms, the circuit disconnects the solar-cell power source from its reservoir capacitor and load, applying a test load (R1) and assessing the resulting voltage drop. If the voltage drops 25% or more, the result is latched into U2 and the power status is provided to the microcontroller.

This ultra-low power circuit draws less than 3 μ A at 1 V. Op amp U1 provides the timer function and controls transistor switches T1 and T2 to apply the test load while simultaneously disconnecting the load. Capacitor C1 temporarily holds the voltage to keep this circuitry and any standby loads powered. Op amp U2 serves as a comparator, tripping when the power source drops more than 25% (with 5% hysteresis). Transistor T3 latches the result, while transistor T4 resets the latch during each assessment period to ensure a fresh reading.


Such test loading is useful for determining the available power from a solar cell, since merely measuring the open circuit voltage generally does not provide an accurate assessment.

2.1. Assessing “Always-On” Circuitry

Generally, an ultra-low-power op amp, like the TS1001, is an excellent option for supporting “always-on” analog circuitry. For example, op amps that are guaranteed to operate under 1 V and consume less than 1 μ A current may be configured as a filter and left continually on, so that a microcontroller making an ADC measurement does not have to stay powered on while the filter settles.

In conclusion, ultra-low-power op amps are useful in low-power solar systems to assess the available power from solar cells before a load is applied, and generally to support standby, “always-on” circuitry, while drawing negligible currents.

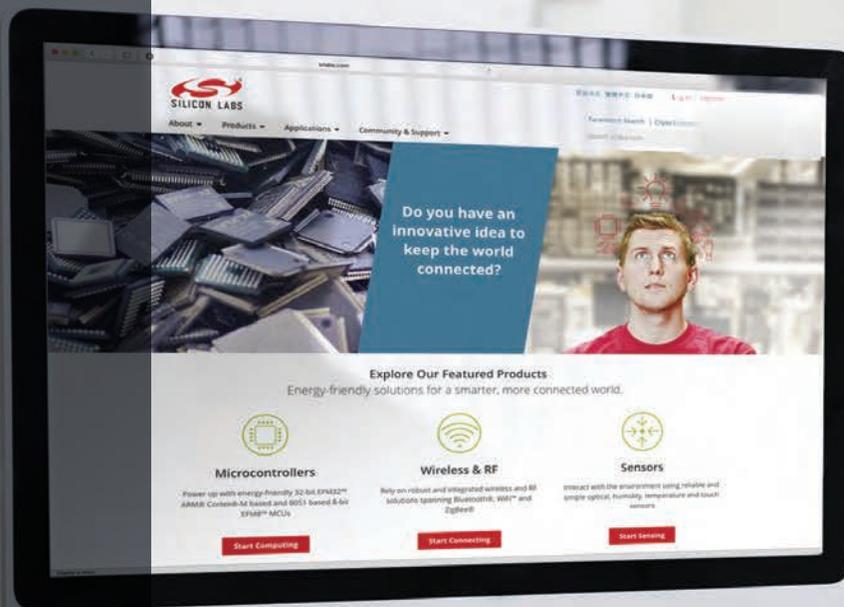
For additional information, see the documentation for the TS1001 or contact Silicon Labs.



Smart.
Connected.
Energy-Friendly



Products
www.silabs.com/products

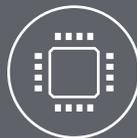

Quality
www.silabs.com/quality



Support and Community
community.silabs.com

Disclaimer

Silicon Laboratories intends to provide customers with the latest, accurate, and in-depth documentation of all peripherals and modules available for system and software implementers using or intending to use the Silicon Laboratories products. Characterization data, available modules and peripherals, memory sizes and memory addresses refer to each specific device, and "Typical" parameters provided can and do vary in different applications. Application examples described herein are for illustrative purposes only. Silicon Laboratories reserves the right to make changes without further notice and limitation to product information, specifications, and descriptions herein, and does not give warranties as to the accuracy or completeness of the included information. Silicon Laboratories shall have no liability for the consequences of use of the information supplied herein. This document does not imply or express copyright licenses granted hereunder to design or fabricate any integrated circuits. The products must not be used within any Life Support System without the specific written consent of Silicon Laboratories. A "Life Support System" is any product or system intended to support or sustain life and/or health, which, if it fails, can be reasonably expected to result in significant personal injury or death. Silicon Laboratories products are generally not intended for military applications. Silicon Laboratories products shall under no circumstances be used in weapons of mass destruction including (but not limited to) nuclear, biological or chemical weapons, or missiles capable of delivering such weapons.

Trademark Information

Silicon Laboratories Inc., Silicon Laboratories, Silicon Labs, SiLabs and the Silicon Labs logo, CMEMS®, EFM, EFM32, EFR, Energy Micro, Energy Micro logo and combinations thereof, "the world's most energy friendly microcontrollers", Ember®, EZLink®, EZMac®, EZRadio®, EZRadioPRO®, DSPLL®, ISOmodem®, Precision32®, ProSLIC®, SiPHY®, USBXpress® and others are trademarks or registered trademarks of Silicon Laboratories Inc. ARM, CORTEX, Cortex-M3 and THUMB are trademarks or registered trademarks of ARM Holdings. Keil is a registered trademark of ARM Limited. All other products or brand names mentioned herein are trademarks of their respective holders.



Silicon Laboratories Inc.
400 West Cesar Chavez
Austin, TX 78701
USA

<http://www.silabs.com>